

16 bit microprocessor report Report



UPPSALA
UNIVERSITET

date: April 29, 2022
author: Yuzhi Chen
course: Digital Electronics Design with VHDL

Abstract

The project task is to design a 16 bit microprocessor kernel using fetch and execute states with ADD, STORE, LOAD, JUMP and JNEG functions.

The final design contains three test cases which are both simulated on software and implemented on hardware using *DE1_SOC* board.

Contents

1	Introduction	1
2	Project Description	1
2.1	Tools Software	1
2.2	Design	1
3	Theory	2
3.1	The design of state machine	2
3.2	The design of bit instructions	2
4	Implementation	3
4.1	Control Unit	3
4.2	Program Counter	4
4.3	Memory Interface	5
4.4	Instruction Register	6
4.5	Accumulator register	7
4.6	Arithmetic Logic Unit	10
4.7	Memory	10
4.8	Clock Frequency Divider	11
4.9	Hex Display	12
4.10	Complete Design	13
5	Tests Result	13
5.1	A=B+C	13
5.2	If AC<0 then PC <= address	14
5.3	If A>=0 then B=C	15
6	Conclusions and evaluation	16
7	Appendix A. Source Code	16
7.1	Control Unit	16
7.2	Program Counter	17
7.3	Memory Interface	18
7.4	Instruction Register	19
7.5	Accumulator register	20
7.6	Arithmetic Logic Unit	21
7.7	Memory	22
7.8	Clock Frequency Divider	23
7.9	Hex Display	24

1 Introduction

This project gives the possibility of building up a basic microprocessor with Program Counter (PC), Instruction Register (IR), Accumulator Register (AC), Arithmetic Logic Unit (ALU), Memory Interface (MIF). The processor is connected to a Memory which stores instructions and values and a hex-display to show the output of Accumulator register. Instructions are 16 bits with 8 bits op code and 8 bits address part pointing on data or the next operation.

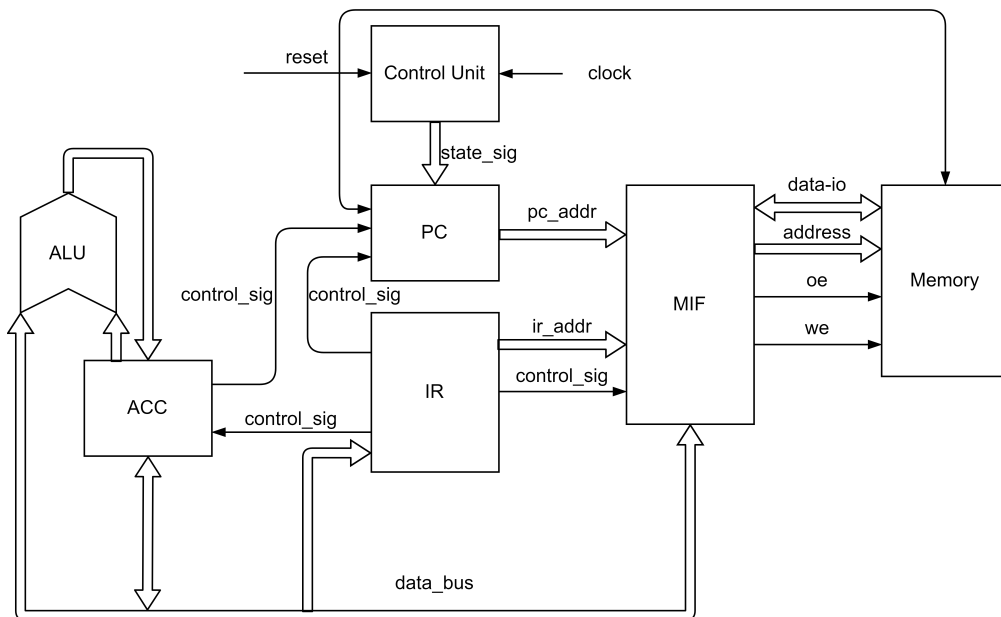


Figure 1.1: Structure of 16 bit microprocessor

The project also gives a good and valuable knowledge about design of state machine and timing issue in hardware programming.

2 Project Description

2.1 Tools Software

The project task is to design a microprocessor kernel that in the end should be tested in hardware. The Quartus project is using a CYCLONE V: 5CSEMA5F31C6.

The Intel Quartus Prime Design Software used to design for Intel FPGAs, SoCs, and complex programmable logic device (CPLD) from design entry and synthesis to optimization, verification, and simulation. ModelSim simulates behavioral, RTL, and gate-level code - delivering increased design quality and debug productivity with platform-independent compile. Single Kernel Simulator technology enables transparent mixing of VHDL and Verilog in one design. The SignalTap Logic Analyzer helps debug an FPGA design by probing the state of the internal signals in the design without the use of external equipment. Defining custom trigger-condition logic provides greater accuracy and improves the ability to isolate problems.

2.2 Design

The design is using smaller components, these units are: Clock Frequency Divider: generate low frequency clock signal Control Unit: control the state machine Program Counter (PC): locate present address Instruction Register (IR): decode and execute Accumulator register (AC): store immediate results Arithmetic Logic Unit (ALU): arithmetic operations Memory Interface (MIF): access memory and data bus Hex Display: display the value of Accumulator register (AC) These units perform

simple tasks that together as a microprocessor that are doing intended operations with a sequence of instructions.

3 Theory

3.1 The design of state machine

The Control Units contains a state machine with two states fetch and execute.

When fetch state, the program counter (PC) keeps the address of the running instruction and do a instruction-fetch. After a successful fetch the program counter is increased by '1'. instruction is found at the address in Memory and go through the memory interface (MIF). The memory interface (MIF) push the value in buswire and then the value is loaded in the instruction register (IR) where the decode will happen. The fetch state can be described that way in microcode like

MIF = PC
 Read memory, (Instruction from memory)
 IR = memory bus
 PC=PC+1

When execute state, The decoding of the instruction part in IR leads to the execution of operations on different registers and the arithmetic logic unit. New data is found in address and push into buswire so the accumulator (AC) which is the primary intermediate storage register and the arithmetic logic unit (ALU) for operations can use them . The execute state can be described that way in microcode like

Decode the op-code to find next state
 MIF=IR
 Start a memory read

 


Figure 3.1: State machine design

3.2 The design of bit instructions

The memory and data parts should then be 16 bits wide. The 8 bits op-code leads to an operation when it is decoded in a control unit. The 8 bits address part is pointing on data or the next operation.

 


Figure 3.2: Data instruction design

The decode table of op code is as follows.

			op-code
ADD	address	$AC \leq AC + \text{contentatthememoryaddress}$	00
STORE	address	$\text{contentatthememoryaddress} \leq AC$	01
LOAD	address	$AC \leq \text{contentatthememoryaddress}$	02
JUMP	address	$PC \leq \text{address}$	03
JNEG	address	$\text{if } AC < 0 \text{ then } PC \leq \text{address}$	04

4 Implementation

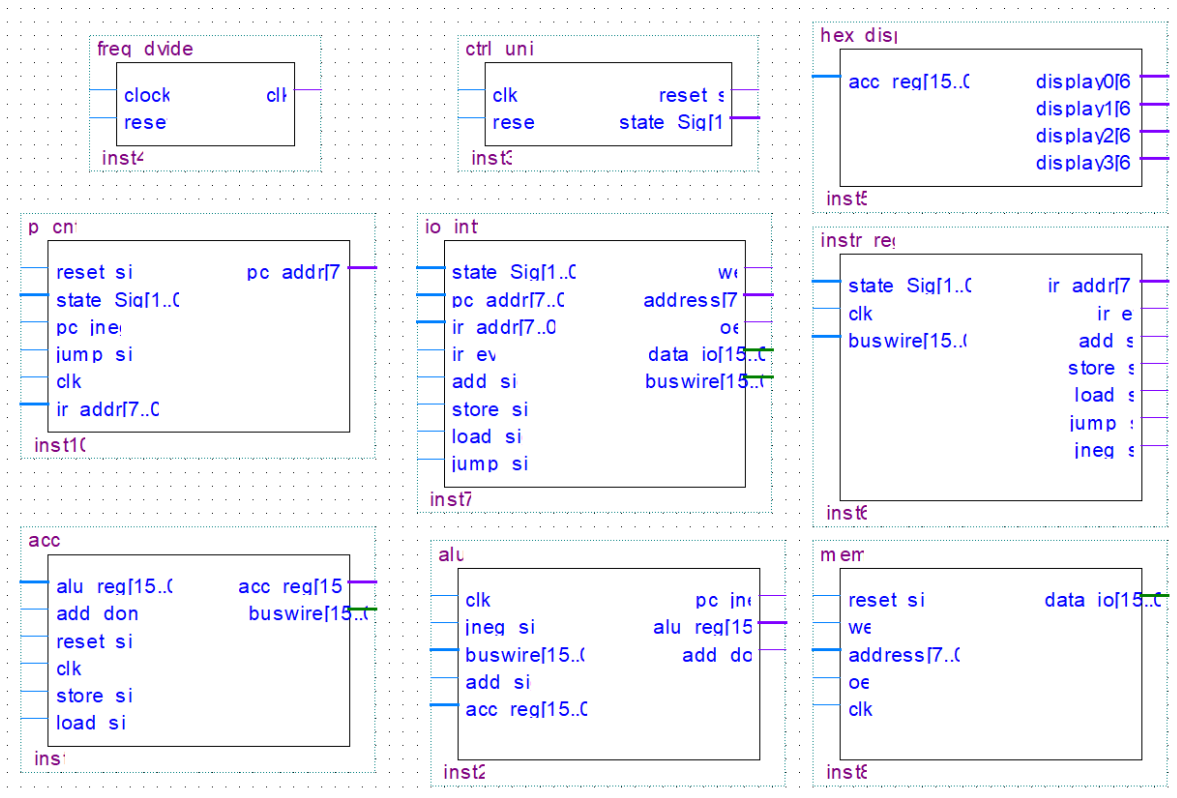


Figure 4.1: All units in this design

4.1 Control Unit

The control Unit viewed as a component has 2 inputs and 2 outputs.

Pins	Type	bits	description
clk	Input	1	clock signal
reset	Input	1	reset button input
reset-sig	Output	1	reset signal
state-sig	Output	2	state signal

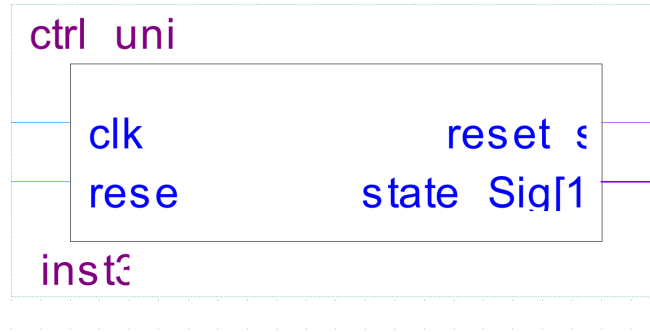


Figure 4.2: Control Unit block

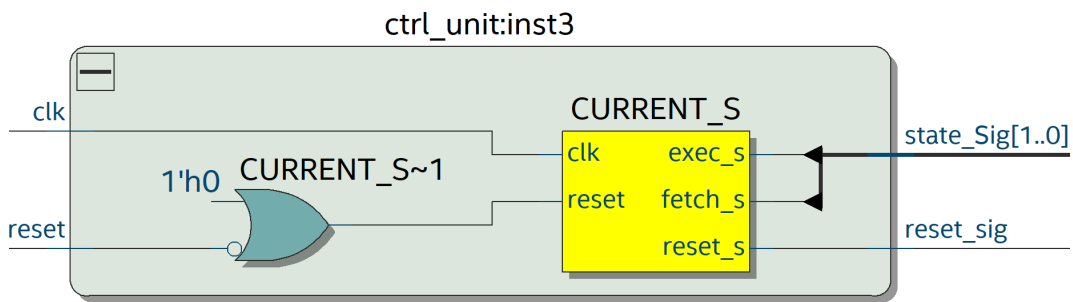


Figure 4.3: Control Unit RTL

4.2 Program Counter

The Program Counter viewed as a component has 6 inputs and 1 output.

Pins	Type	bits	description
reset-sig	Input	1	reset signal
state-sig	Input	2	state signal
pc-jneg	Input	1	do JNEG when receive signal
jump-sig	Input	1	do JUMP when receive signal
clk	Input	1	clock signal
ir-addr	Input	8	address from IR
pc-addr	Output	8	address to MIF

 


Figure 4.4: Program Counter block

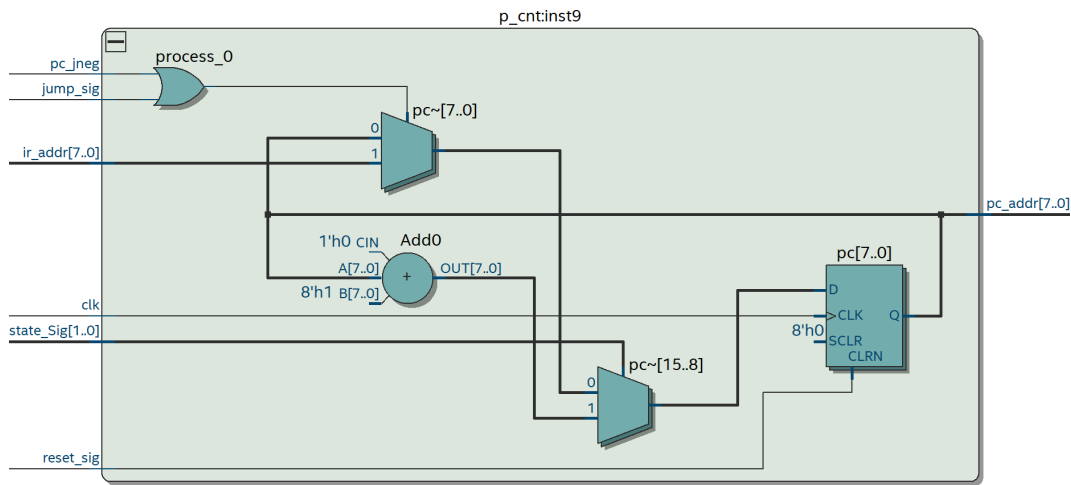


Figure 4.5: Program Counter RTL

4.3 Memory Interface

The Memory Interface viewed as a component has 8 inputs and 5 outputs.

Pins	Type	bits	description
state-sig	Input	2	state signal
pc-addr	Input	8	address from PC
ir-addr	Input	8	address from IR
ir-ev	Input	1	switch the address between IR and PC
add-sig	Input	1	push value to bus when receive signal
store-sig	Input	1	push value to Memory when receive signal
load-sig	Input	1	push value to bus when receive signal
jump-sig	Input	1	push value to bus when receive signal
we	Output	1	writing enable
address	Output	8	address to Memory
oe	Output	1	Output enable
data-io	Input/Output	16	databus between MIF and Memory
buswire	Input/Output	16	databus in microprocessor

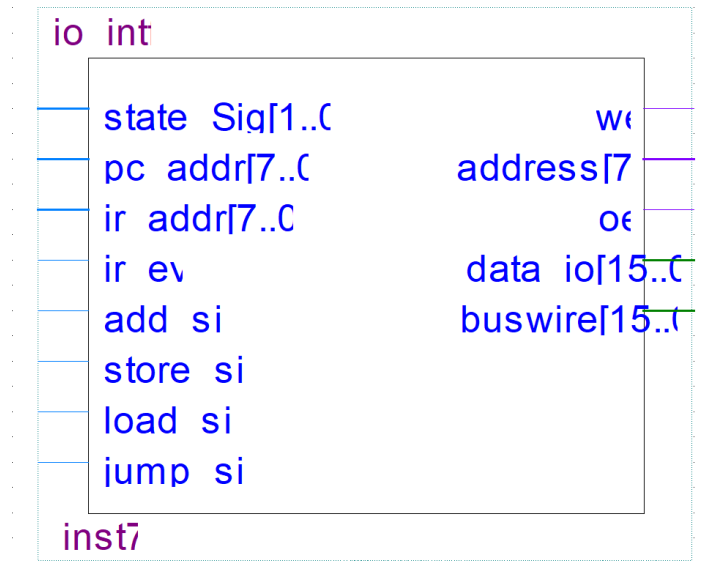


Figure 4.6: Memory Interface block

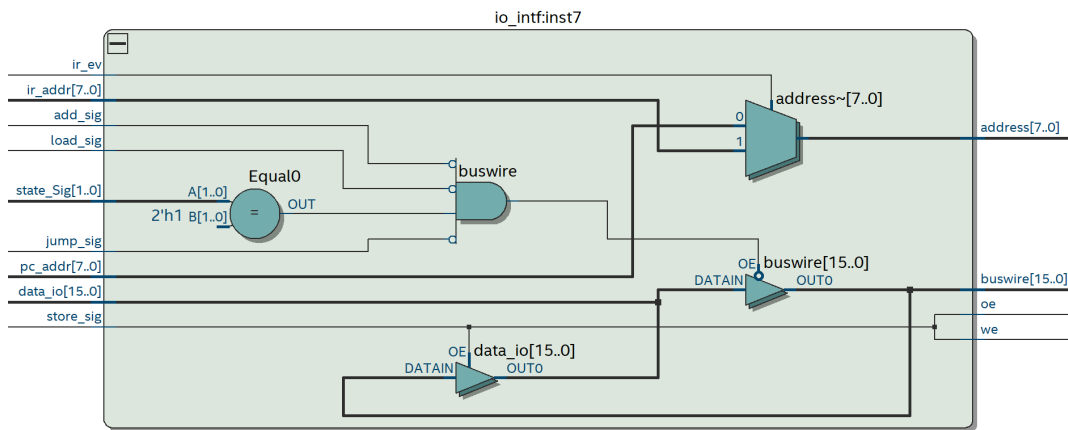


Figure 4.7: Memory Interface RTL

4.4 Instruction Register

The Instruction Register viewed as a component has 3 inputs and 7 outputs.

Pins	Type	bits	description
state-sig	Input	2	state signal
clk	Input	1	clock signal
buswire	Input	16	databus in microprocessor
ir-addr	Output	8	address to MIF
ir-ev	Output	1	switch the address between IR and PC
add-sig	Output	1	operation ADD
store-sig	Output	1	operation STORE
load-sig	Output	1	operation LOAD
jump-sig	Output	1	operation JUMP
jneg-sig	Output	1	operation JNEG

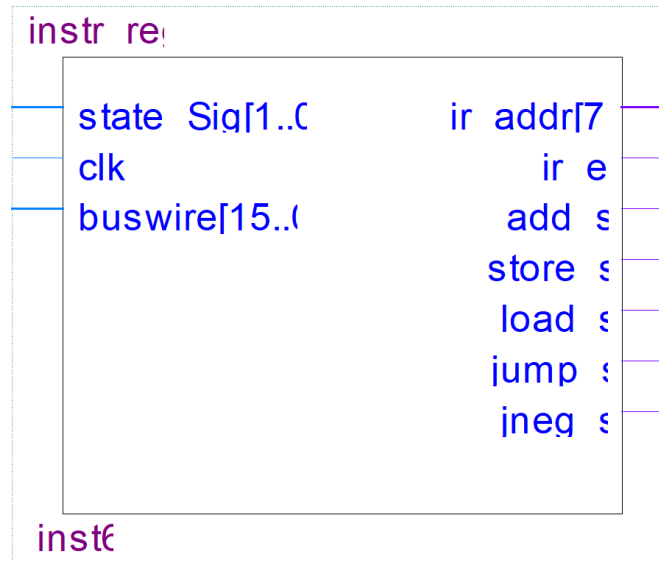


Figure 4.8: Instruction Register block

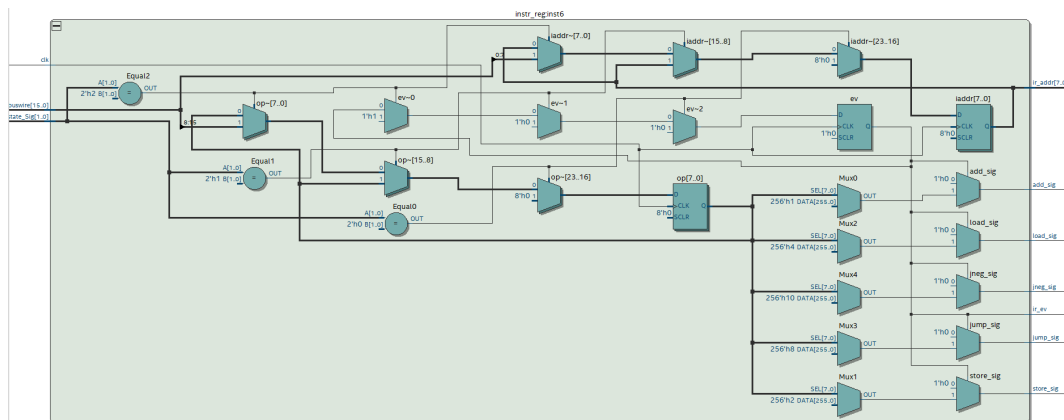


Figure 4.9: Instruction Register RTL

4.5 Accumulator register

The Accumulator viewed as a component has 6 inputs and 2 outputs.

Pins	Type	bits	description
alu-reg	Input	16	data from ALU
add-done	Input	1	get ALU value when receive signal
reset-sig	Input	1	reset ACC to 0
clk	Input	1	clock signal
store-sig	Input	1	wrtie value to bus
load-sig	Input	1	load value from bus
acc-reg	Output	16	data to ALU
buswire	Input/Output	16	databus in microprocessor

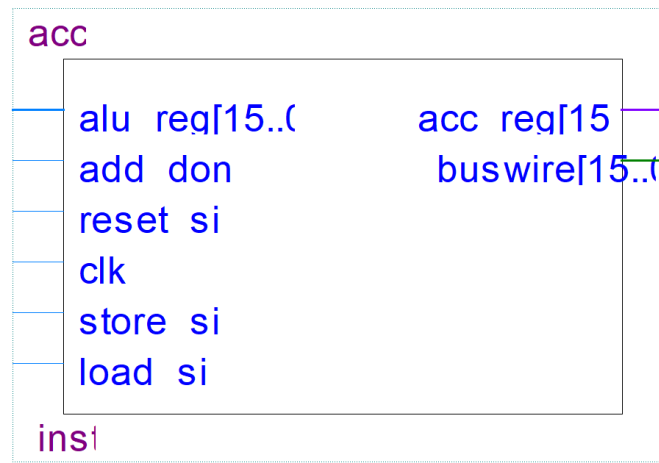


Figure 4.10: Accumulator register block

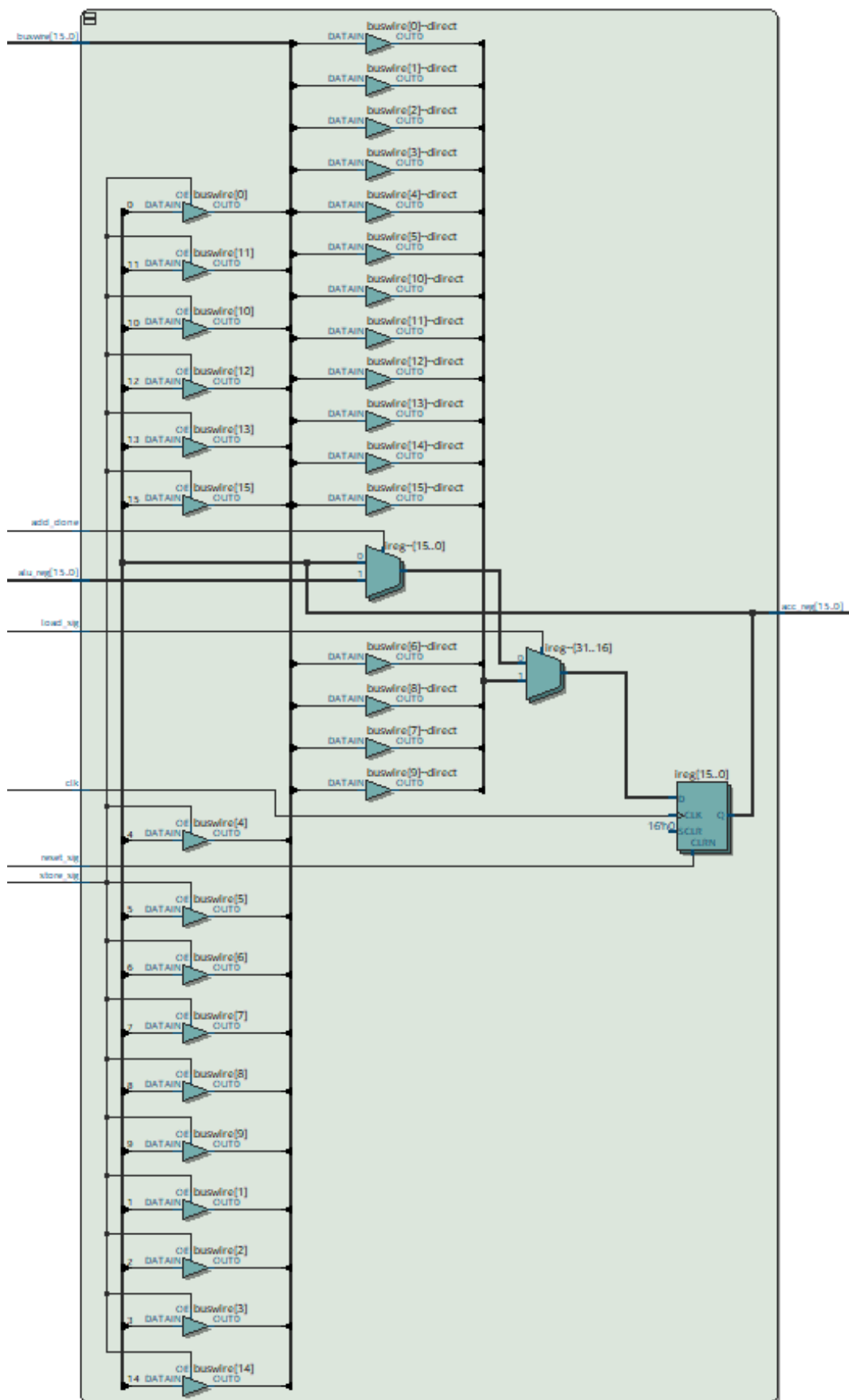


Figure 4.11: Accumulator register RTL

4.6 Arithmetic Logic Unit

The Arithmetic Logic Unit viewed as a component has 5 inputs and 3 outputs.

Pins	Type	bits	description
clk	Input	1	clock signal
jneg-sig	Input	1	do JENG operation
buswire	Input	16	databus in microprocessor
add-sig	Input	1	do ADD operation
acc-reg	Input	16	data from ACC
pc-jneg	Input	1	tell PC do JENG operation
alu-reg	Output	16	data to ACC
add-done	Output	1	tell ACC add complete

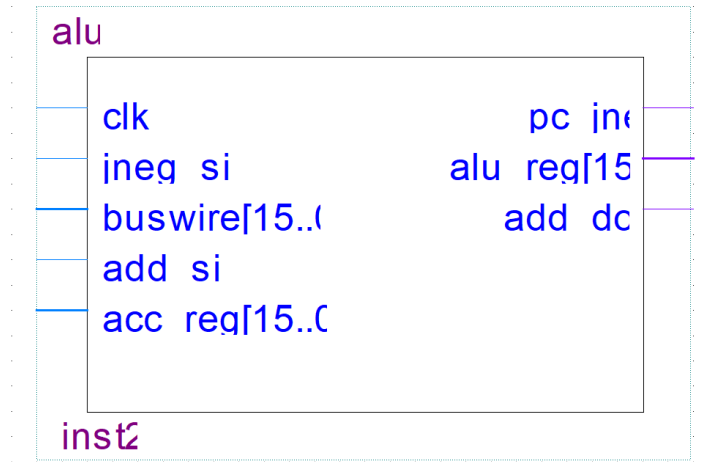


Figure 4.12: Arithmetic Logic Unit block

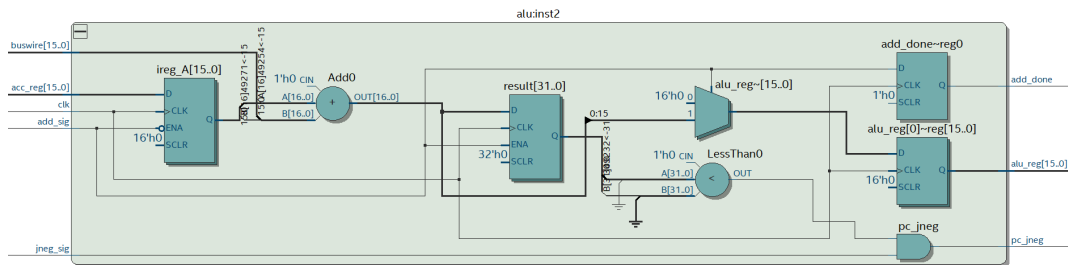


Figure 4.13: Arithmetic Logic Unit RTL

4.7 Memory

The Memory viewed as a component has 5 inputs and 1 output.

Pins	Type	bits	description
reset-sig	Input	1	reset Memory to preset value
we	Input	1	write enable
address	Input	8	address from MIF
oe	Input	1	output enable
clk	Input	1	clock signal
data-io	Input/Output	16	databus between MIF and Memory

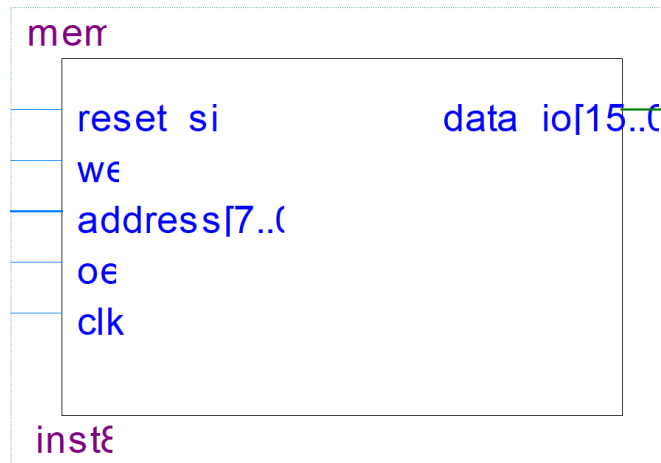


Figure 4.14: Memory block

 


Figure 4.15: Memory RTL

4.8 Clock Frequency Divider

The Clock Frequency Divider viewed as a component has 2 inputs and 1 output.

Pins	Type	bits	description
clock	Input	1	high frequency clock signal
reset	Input	1	reset button input
clk	Input	1	low frequency clock signal

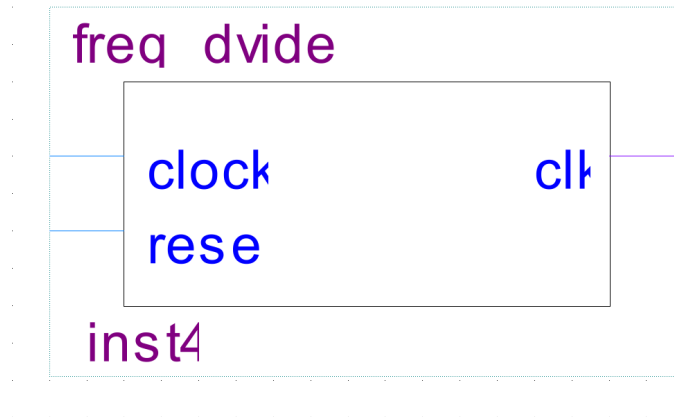


Figure 4.16: Clock Frequency Divider block

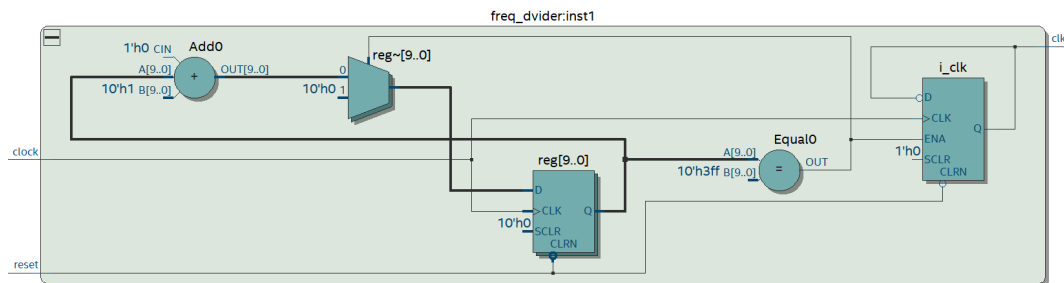


Figure 4.17: Clock Frequency Divider RTL

4.9 Hex Display

The Hex Display viewed as a component has 1 input and 4 outputs.

Pins	Type	bits	description
acc-reg	Input	16	data from ACC
display0-3	Output	1	decoded hex signal



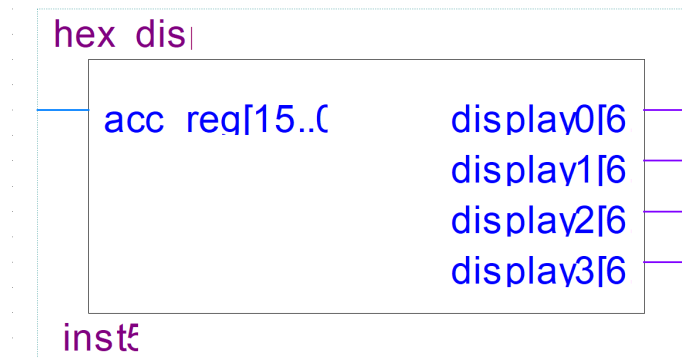


Figure 4.18: Hex Display block

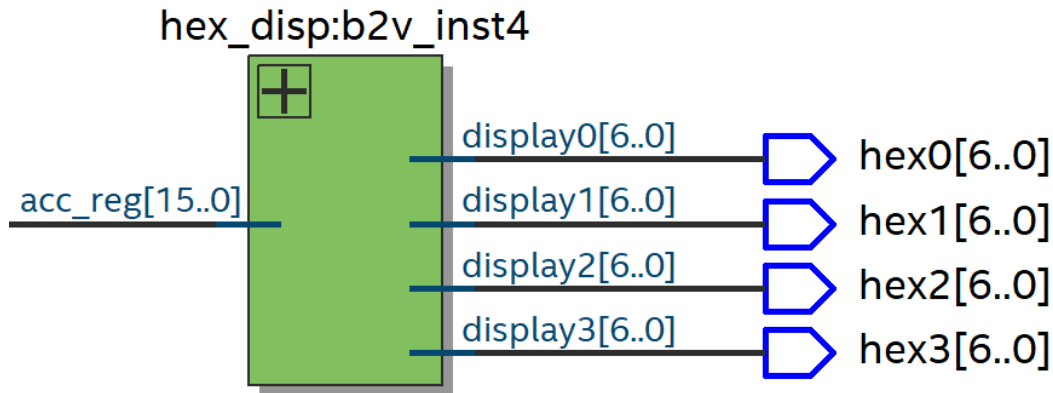

4.10 Complete Design

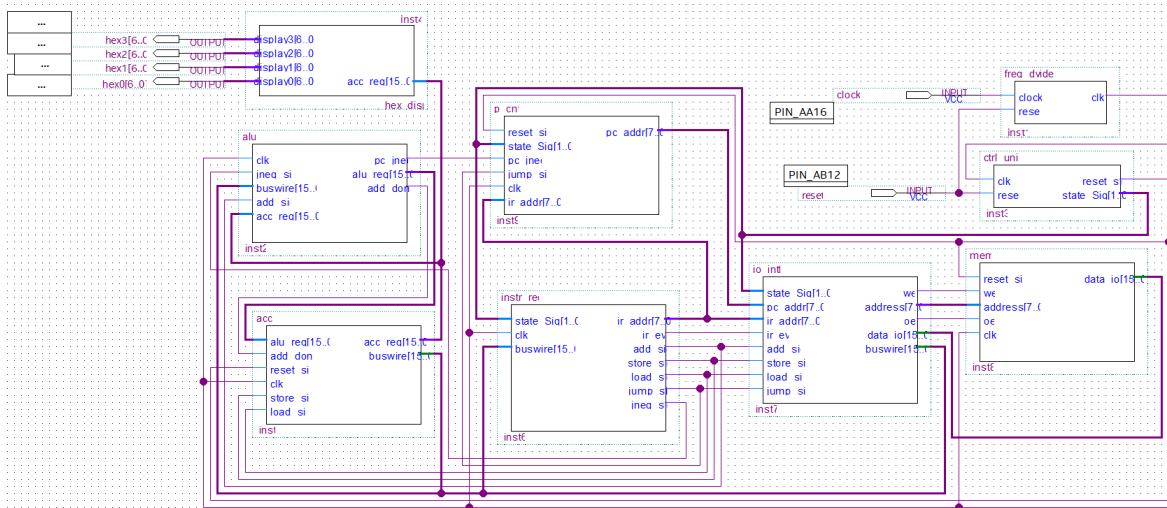

5 Tests Result

Figure 5.1 shows the code for 'A=B+C' process.

4. `mem-array(3) >= "0000001011111111"; -02FF:LOAD 255`
Load the value in `mem-array(255)`, ACC should contains a value 7 now. It is used to check if value is loaded in `mem-array(255)`.
5. `mem-array(4) >= "0000001100000100"; -0304:JUMP 04`
PC should jump to 04, which means this instruction will execute infinitely. ACC should hold the value 7.

Figure 5.1: A=B+C Code

Figure 5.2: RTL simulation of the test case

Figure 5.3: SignalTap of the test case

Figure 5.4 shows the code for 'If $AC < 0$ then $PC \leq \text{address}$ ' process.

4. mem-array(3) >= "0000001011111110"; -02FE:LOAD 254
In this case this instruction should be skipped and ACC should contains a value -1.
5. mem-array(4) >= "0000001100000100"; -0304:JUMP 04
PC should jump to 04, which means this instruction will execute infinitely. ACC should hold the value -1.

```

mem_array(0) <= "0000001011111110";  --02FE:LOAD 254
mem_array(1) <= "0000000011111101";  --00FD:ADD 253
mem_array(2) <= "0000010000000100";  --0404:JNEG 04
mem_array(3) <= "0000001011111110";  --02FE:LOAD 254
mem_array(4) <= "0000001100000100";  --0304:JUMP 04
mem_array(253) <= "111111111111011";  -- -4
mem_array(254) <= "000000000000011";  -- 3

```

Figure 5.4: If AC<0 then PC <= address Code

 


Figure 5.5: RTL simulation of the test case

 


Figure 5.6: SignalTap of the test case

5.3 If A>=0 then B=C

Figure 5.4 shows the code for 'If A>=0 then B=C' process.

1. mem-array(0) >= "0000001011111110"; -02FE:LOAD 254
Load the value in mem-array(254), ACC should contains a value 3 now.
2. mem-array(1) >= "0000000011111101"; -00FD:ADD 253
Add the value in mem-array(253), ACC should contains a value 7 now.
3. mem-array(2) >= "0000010000000100"; -0404:JNEG 04
Rise a JNEG process. In this case, PC will not jump.
4. mem-array(3) >= "0000001011111110"; -02FE:LOAD 254
Load the value in mem-array(254), ACC should contains a value 3 now.

5. mem_array(4) >= "0000001100000100"; -0304:JUMP 04
 PC should jump to 04, which means this instruction will execute infinitely. ACC should hold the value 3.

```

mem_array(0) <= "0000001011111110"; --02FE:LOAD 254
mem_array(1) <= "0000000011111101"; --00FD:ADD 253
mem_array(2) <= "0000010000000100"; --0404:JNEG 04
mem_array(3) <= "0000001011111110"; --02FE:LOAD 254
mem_array(4) <= "0000001100000100"; --0304:JUMP 04
mem_array(253) <= "0000000000000100"; -- 4
mem_array(254) <= "0000000000000011"; -- 3

```

Figure 5.7: If A>=0 then B=C Code

 


Figure 5.8: RTL simulation of the test case

 


Figure 5.9: SignalTap of the test case

6 Conclusions and evaluation

By analyzing the RTL waveform and signaltap waveform, it can be seen that the microprocessor has obtained the correct result at the RTL simulation level and SignalTap simulation. The project eventually shows correct value and is able to pass all three test case on hardware.

From figure5.3 figure5.6 figure5.9, the SignalTap waveform cannot show the first few clock cycle of the wave. It can only show the final wave in the infinite loop.

Through many experiments and analysis, I found the problem might be that the setting of SignalTap trigger is not correct.

7 Appendix A. Source Code

7.1 Control Unit

```

1  LIBRARY ieee;
2  USE ieee.std_logic_1164.ALL;
3
4  ENTITY ctrl_unit IS
5      PORT(
6          clk: IN std_logic ;
7          reset: IN std_logic ;
8          reset_sig: OUT std_logic;
9          state_Sig: OUT std_logic_vector(1 DOWNTO 0) --state signal
10     );
11 END ctrl_unit;
12
13 ARCHITECTURE ctrl_unit_architecture OF ctrl_unit IS
14     TYPE state_type IS ( reset_s , fetch_s , exec_s); --define state type
15     SIGNAL CURRENT_S,NEXT_S: state_type;
16     SIGNAL iev: std_logic ;
17 BEGIN
18
19     PROCESS(reset, clk)
20     BEGIN
21         IF reset = '0' THEN
22             CURRENT_S <= reset_s; --reset the state machine
23         ELSIF rising_edge(clk) THEN
24             CURRENT_S <= NEXT_S;
25         END IF;
26     END PROCESS;
27
28     PROCESS(CURRENT_S)
29     BEGIN
30         reset_sig <= '0';
31         CASE CURRENT_S IS
32             WHEN reset_s => --reset state
33                 NEXT_S <= fetch_s;
34                 state_Sig <= "00";
35                 reset_sig <= '1';
36
37             WHEN fetch_s => --fetch state
38                 NEXT_S <= exec_s;
39                 state_Sig <= "10";
40
41             WHEN exec_s => --execute state
42                 NEXT_S <= fetch_s;
43                 state_Sig <= "01";
44
45             WHEN OTHERS =>
46                 state_Sig <= "XX";
47             END CASE;
48         END PROCESS;
49
50 END ctrl_unit_architecture ;

```

7.2 Program Counter

```

1  LIBRARY ieee;
2  USE ieee.std_logic_1164.ALL;

```

```

3  USE ieee. std_logic_unsigned .ALL;
4
5  ENTITY p_cnt IS
6      PORT(
7          reset_sig : IN  std_logic ;
8          state_Sig : IN  std_logic_vector (1 DOWNT0 0);
9          pc_jneg : IN  std_logic ;
10         jump_sig : IN  std_logic ;
11         clk : IN  std_logic ;
12         ir_addr : IN  std_logic_vector (7 DOWNT0 0);
13         pc_addr : OUT std_logic_vector(7 DOWNT0 0)
14     );
15 END p_cnt;
16
17 ARCHITECTURE p_cnt_architecture OF p_cnt IS
18     SIGNAL pc : std_logic_vector (7 DOWNT0 0);
19 BEGIN
20
21     PROCESS(clk,reset_sig)
22     BEGIN
23         IF reset_sig = '1' THEN --reset program counter
24             pc <= "00000000";
25         ELSIF rising_edge (clk) THEN
26             IF state_Sig (1) = '1' THEN --pc add 1 when exec_s
27                 pc <= pc + '1';
28             ELSIF jump_sig='1' OR pc_jneg='1' THEN --pc jump
29                 pc <= ir_addr;
30             END IF;
31         END IF;
32     END PROCESS;
33     pc_addr <= pc; --give address to MIF
34
35 END p_cnt_architecture;

```

7.3 Memory Interface

```

1  LIBRARY ieee;
2  USE ieee. std_logic_1164 .ALL;
3  USE ieee. std_logic_unsigned .ALL;
4
5  ENTITY io_intf IS
6      PORT(
7          state_Sig : IN  std_logic_vector (1 DOWNT0 0);
8          pc_addr : IN  std_logic_vector (7 DOWNT0 0); --address from pc
9          ir_addr : IN  std_logic_vector (7 DOWNT0 0); --address from ir
10         ir_ev : IN  std_logic ;
11         add_sig : IN  std_logic ;
12         store_sig : IN  std_logic ;
13         load_sig : IN  std_logic ;
14         jump_sig : IN  std_logic ;
15         we : OUT std_logic; --write enable
16         address : OUT std_logic_vector(7 DOWNT0 0);
17         oe : OUT std_logic; --output enable
18         data_io : INOUT std_logic_vector(15 DOWNT0 0);
19         buswire : INOUT std_logic_vector(15 DOWNT0 0)
20     );

```

```

21 END io_intf;
22
23 ARCHITECTURE io_intf_architecture OF io_intf IS
24 BEGIN
25
26     buswire <= (OTHERS=>'Z') WHEN state_sig="01" AND jump_sig='0' AND load_sig='0' AND
        add_sig='0' ELSE data_io;
27     --output to MEMORY
28     address <= ir_addr WHEN ir_ev='1' ELSE pc_addr;
29     data_io <= buswire WHEN store_sig='1' ELSE (OTHERS=>'Z');
30     PROCESS(store_sig)
31     BEGIN
32         IF store_sig='1' THEN --output to MEMORY
33             we <= '1';
34             oe <= '1';
35         ELSE
36             we <= '0';
37             oe <= '0';
38         END IF;
39     END PROCESS;
40
41 END io_intf_architecture ;

```

7.4 Instruction Register

```

1  LIBRARY ieee;
2  USE ieee.std_logic_1164.ALL;
3  USE ieee.std_logic_unsigned.ALL;
4
5  ENTITY instr_reg IS
6      PORT(
7          state_sig : IN std_logic_vector (1 DOWNTO 0);
8          clk : IN std_logic ;
9          buswire: IN std_logic_vector (15 DOWNTO 0);
10         ir_addr : OUT std_logic_vector(7 DOWNTO 0);
11         ir_ev : OUT std_logic;
12         add_sig: OUT std_logic;
13         store_sig : OUT std_logic;
14         load_sig : OUT std_logic;
15         jump_sig: OUT std_logic;
16         jneg_sig : OUT std_logic
17     );
18 END instr_reg;
19
20 ARCHITECTURE instr_reg_architecture OF instr_reg IS
21 SIGNAL op: std_logic_vector (7 DOWNTO 0);
22 SIGNAL iaddr: std_logic_vector (7 DOWNTO 0);
23 SIGNAL ev: std_logic;
24 SIGNAL decode_done: std_logic := '0';
25 BEGIN
26
27     --output to MIF
28     ir_addr <= iaddr;
29     ir_ev <= decode_done;
30
31     PROCESS(clk)

```

```

32 BEGIN
33     IF rising_edge (clk) THEN
34         IF state_Sig = "00" THEN --reset_s
35             ev <= '0';
36             iaddr <= (OTHERS=>'0');
37             op <= (OTHERS=>'0');
38         ELSIF state_Sig = "01" THEN --fetch_s
39             ev <= '0';
40         ELSIF state_Sig = "10" THEN --execute_s
41             ev <= '1';
42             iaddr <= buswire(7 DOWNT0 0); --get address
43             op <= buswire(15 DOWNT0 8); --get op code
44         END IF;
45     END IF;
46 END PROCESS;
47
48 PROCESS(ev) --decode process
49 BEGIN
50     add_sig <= '0'; --reset output signal
51     store_sig <= '0';
52     load_sig <= '0';
53     jump_sig <= '0';
54     jneg_sig <= '0';
55     decode_done <= '0';
56     IF ev='1' THEN
57         decode_done <= '1';
58         CASE op IS
59             WHEN "00000000" => --ADD
60                 add_sig <= '1';
61             WHEN "00000001" => --STORE
62                 store_sig <= '1';
63             WHEN "00000010" => --LOAD
64                 load_sig <= '1';
65             WHEN "00000011" => --JUMP
66                 jump_sig <= '1';
67             WHEN "00000100" => --JNEG
68                 jneg_sig <= '1';
69             WHEN OTHERS =>
70                 NULL;
71         END CASE;
72     END IF;
73 END PROCESS;
74 END instr_reg_architecture ;

```

7.5 Accumulator register

```

1  LIBRARY ieee;
2  USE ieee.std_logic_1164.ALL;
3  USE ieee.std_logic_unsigned.ALL;
4
5  ENTITY acc IS
6      PORT(
7          alu_reg: IN std_logic_vector (15 DOWNT0 0);
8          add_done: IN std_logic ;
9          reset_sig : IN std_logic ;
10         clk: IN std_logic ;

```

```

11         store_sig : IN std_logic ;
12         load_sig : IN std_logic ;
13         acc_reg : OUT std_logic_vector(15 DOWNTO 0);
14         buswire: INOUT std_logic_vector(15 DOWNTO 0)
15     );
16 END acc;
17
18 ARCHITECTURE acc_architecture OF acc IS
19 SIGNAL ireg: std_logic_vector (15 DOWNTO 0);
20 BEGIN
21
22     acc_reg <= ireg; --output to ALU
23     buswire <= ireg WHEN store_sig='1' ELSE (OTHERS=>'Z'); --write to buswire
24
25     PROCESS(clk,reset_sig)
26     BEGIN
27         IF reset_sig = '1' THEN
28             ireg <= "0000000000000000";
29         ELSIF rising_edge (clk) THEN
30             IF load_sig='1' THEN
31                 ireg <= buswire; --get content at memory address
32             ELSIF add_done='1' THEN
33                 ireg <= alu_reg; --refresh when ADD complete
34             END IF;
35         END IF;
36     END PROCESS;
37
38 END acc_architecture;

```

7.6 Arithmetic Logic Unit

```

1  LIBRARY ieee;
2  USE ieee.std_logic_1164.ALL;
3  USE ieee.std_logic_signed.ALL;
4
5  ENTITY alu IS
6      PORT(
7          clk: IN std_logic ;
8          jneg_sig : IN std_logic ;
9          buswire: IN std_logic_vector (15 DOWNTO 0);
10         add_sig: IN std_logic ;
11         pc_jneg: OUT std_logic;
12         acc_reg: IN std_logic_vector (15 DOWNTO 0);
13         alu_reg: OUT std_logic_vector(15 DOWNTO 0);
14         add_done: OUT std_logic
15     );
16 END alu;
17
18 ARCHITECTURE alu_architecture OF alu IS
19 SIGNAL ireg_A: std_logic_vector (15 DOWNTO 0); --from AC
20 BEGIN
21
22     pc_jneg <= '1' WHEN jneg_sig='1' AND conv_integer(alu_reg) < 0 ELSE '0';
23     PROCESS(clk)
24
25     BEGIN

```

```

26     IF rising_edge (clk) THEN
27         IF add_sig='1' THEN --calculation
28             alu_reg <= acc_reg + buswire;
29             add_done <= '1';
30         ELSE
31             ireg_A <= acc_reg; --input from AC
32             alu_reg <= (OTHERS=>'0');
33             add_done <= '0';
34         END IF;
35     END IF;
36 END PROCESS;
37
38 END alu_architecture;

```

7.7 Memory

```

1  LIBRARY ieee;
2  USE ieee.std_logic_1164.ALL;
3
4  PACKAGE MEM256 IS
5      COMPONENT mem IS
6          PORT(
7              reset_sig : IN std_logic ;
8              we: IN std_logic ; --write enable
9              address: IN std_logic_vector (7 DOWNTO 0);
10             oe: IN std_logic ; --output enable
11             clk: IN std_logic ;
12             data_io: INOUT std_logic_vector(15 DOWNTO 0)
13         );
14     END COMPONENT;
15 END PACKAGE MEM256;
16
17
18 LIBRARY ieee;
19 USE ieee.std_logic_1164.ALL;
20 USE ieee.std_logic_unsigned.ALL;
21
22 ENTITY mem IS
23     PORT(
24         reset_sig : IN std_logic ;
25         we: IN std_logic ; --write enable
26         address: IN std_logic_vector (7 DOWNTO 0);
27         oe: IN std_logic ; --output enable
28         clk: IN std_logic ;
29         data_io: INOUT std_logic_vector(15 DOWNTO 0)
30     );
31 END mem;
32
33 ARCHITECTURE mem_architecture OF mem IS
34     TYPE MEMORY IS ARRAY(255 DOWNTO 0) OF std_logic_vector(15 DOWNTO 0);
35     SIGNAL mem_array: MEMORY:=(OTHERS => (OTHERS => '0'));
36     SIGNAL data_in: std_logic_vector (15 DOWNTO 0);
37     SIGNAL data_out: std_logic_vector (15 DOWNTO 0);
38     BEGIN
39
40         data_in <= data_io;

```



```

41 data_io <= data_out WHEN oe='0' ELSE (OTHERS => 'Z');
42 --internal memory structure
43 data_out <= mem_array(conv_integer(address)) WHEN we='0' ELSE (OTHERS => 'Z');
44
45 PROCESS(clk,we,reset_sig) --writing process
46 BEGIN
47     IF reset_sig = '1' THEN
48         --preset value
49         mem_array(0) <= "0000001011111110"; --02FE:LOAD 254
50         mem_array(1) <= "0000010000000100"; --0403:JNEG 04
51         mem_array(2) <= "0000001011111101"; --0304:LOAD 253
52         mem_array(3) <= "0000001100000011"; --0303:JUMP 03
53         mem_array(253) <= "0000000000000100"; --0004
54         mem_array(254) <= "0000000000000011"; --0003
55     ELSIF rising_edge(clk) THEN
56         IF we='1' THEN
57             mem_array(conv_integer(address)) <= data_in;
58         END IF;
59     END IF;
60 END PROCESS;
61
62 END mem_architecture;
63
64
65 LIBRARY ieee;
66 USE ieee.std_logic_1164.ALL;
67 USE work.MEM256.ALL;
68
69 ENTITY my_mem256 IS
70     PORT(
71         reset_sig : IN std_logic ;
72         we: IN std_logic ; --write enable
73         address: IN std_logic_vector (7 DOWNTO 0);
74         oe: IN std_logic ; --output enable
75         clk: IN std_logic ;
76         data_in: IN std_logic_vector (15 DOWNTO 0);
77         data_out: OUT std_logic_vector(15 DOWNTO 0)
78     );
79 END my_mem256;
80
81 ARCHITECTURE my_mem256_architecture OF my_mem256 IS
82     SIGNAL bidirectional_buffer : std_logic_vector (15 downto 0);
83     BEGIN
84
85         data_out <= bidirectional_buffer ;
86         bidirectional_buffer <= data_in WHEN oe='1' ELSE (OTHERS => 'Z');
87         todo: mem port map (reset_sig,we,address,oe,clk, bidirectional_buffer );
88
89     END my_mem256_architecture;

```

7.8 Clock Frequency Divider

```

1 LIBRARY ieee;
2 USE ieee.std_logic_1164.ALL;
3 USE ieee.std_logic_unsigned.ALL;
4

```

```

5 ENTITY freq_dvider IS
6     PORT(
7         clock: IN std_logic ;
8         reset : IN std_logic ;
9         clk: OUT std_logic
10    );
11 END freq_dvider;
12
13 ARCHITECTURE freq_dvider_architecture OF freq_dvider IS
14 SIGNAL reg: INTEGER RANGE 0 TO 24999999;
15 SIGNAL i_clk: std_logic ;
16 BEGIN
17
18     PROCESS(reset,clock)
19     BEGIN
20         IF reset='0' THEN
21             reg <= 0;
22             i_clk <= '0';
23         ELSIF rising_edge(clock) THEN
24             IF reg=24999999 THEN
25                 i_clk <= not i_clk;
26                 reg <= 0;
27             ELSE
28                 reg <= reg + 1;
29             END IF;
30         END IF;
31     END PROCESS;
32
33     clk <= i_clk;
34
35 END freq_dvider_architecture ;

```

7.9 Hex Display

```

1 LIBRARY ieee;
2 USE ieee.std_logic_1164.ALL;
3 USE ieee.std_logic_unsigned.ALL;
4
5 ENTITY hex_disp IS
6     PORT(
7         acc_reg: IN std_logic_vector (15 DOWNT0 0);
8         display0 : OUT std_logic_vector(6 DOWNT0 0);
9         display1 : OUT std_logic_vector(6 DOWNT0 0);
10        display2 : OUT std_logic_vector(6 DOWNT0 0);
11        display3 : OUT std_logic_vector(6 DOWNT0 0)
12    );
13 END hex_disp;
14
15 ARCHITECTURE hex_disp_architecture OF hex_disp IS
16 SIGNAL ori0: std_logic_vector (3 DOWNT0 0);
17 SIGNAL ori1: std_logic_vector (3 DOWNT0 0);
18 SIGNAL ori2: std_logic_vector (3 DOWNT0 0);
19 SIGNAL ori3: std_logic_vector (3 DOWNT0 0);
20 BEGIN
21
22     ori0 <= acc_reg(3 DOWNT0 0);

```

```

23 ori1 <= acc_reg(7 DOWNT0 4);
24 ori2 <= acc_reg(11 DOWNT0 8);
25 ori3 <= acc_reg(15 DOWNT0 12);
26 PROCESS(ori0,ori1,ori2, ori3 )
27 BEGIN
28     CASE ori0 IS
29         WHEN "0000" => display0 <= "0000001"; --0:01
30         WHEN "0001" => display0 <= "1001111"; --1:4F
31         WHEN "0010" => display0 <= "0010010"; --2:12
32         WHEN "0011" => display0 <= "0000110"; --3:06
33         WHEN "0100" => display0 <= "1001100"; --4:4C
34         WHEN "0101" => display0 <= "0100100"; --5:24
35         WHEN "0110" => display0 <= "0100000"; --6:20
36         WHEN "0111" => display0 <= "0001111"; --7:0F
37         WHEN "1000" => display0 <= "0000000"; --8:00
38         WHEN "1001" => display0 <= "0000100"; --9:04
39         WHEN "1010" => display0 <= "0001000"; --A:08
40         WHEN "1011" => display0 <= "1100000"; --B:60
41         WHEN "1100" => display0 <= "0110001"; --C:31
42         WHEN "1101" => display0 <= "1000010"; --D:42
43         WHEN "1110" => display0 <= "0110000"; --E:30
44         WHEN "1111" => display0 <= "0111000"; --F:38
45         WHEN OTHERS => display0 <= "0000000";
46     END CASE;
47
48     CASE ori1 IS
49         WHEN "0000" => display1 <= "0000001"; --0:01
50         WHEN "0001" => display1 <= "1001111"; --1:4F
51         WHEN "0010" => display1 <= "0010010"; --2:12
52         WHEN "0011" => display1 <= "0000110"; --3:06
53         WHEN "0100" => display1 <= "1001100"; --4:4C
54         WHEN "0101" => display1 <= "0100100"; --5:24
55         WHEN "0110" => display1 <= "0100000"; --6:20
56         WHEN "0111" => display1 <= "0001111"; --7:0F
57         WHEN "1000" => display1 <= "0000000"; --8:00
58         WHEN "1001" => display1 <= "0000100"; --9:04
59         WHEN "1010" => display1 <= "0001000"; --A:08
60         WHEN "1011" => display1 <= "1100000"; --B:60
61         WHEN "1100" => display1 <= "0110001"; --C:31
62         WHEN "1101" => display1 <= "1000010"; --D:42
63         WHEN "1110" => display1 <= "0110000"; --E:30
64         WHEN "1111" => display1 <= "0111000"; --F:38
65         WHEN OTHERS => display1 <= "0000000";
66     END CASE;
67
68     CASE ori2 IS
69         WHEN "0000" => display2 <= "0000001"; --0:01
70         WHEN "0001" => display2 <= "1001111"; --1:4F
71         WHEN "0010" => display2 <= "0010010"; --2:12
72         WHEN "0011" => display2 <= "0000110"; --3:06
73         WHEN "0100" => display2 <= "1001100"; --4:4C
74         WHEN "0101" => display2 <= "0100100"; --5:24
75         WHEN "0110" => display2 <= "0100000"; --6:20
76         WHEN "0111" => display2 <= "0001111"; --7:0F
77         WHEN "1000" => display2 <= "0000000"; --8:00
78         WHEN "1001" => display2 <= "0000100"; --9:04

```

```

79      WHEN "1010" => display2 <= "0001000"; --A:08
80      WHEN "1011" => display2 <= "1100000"; --B:60
81      WHEN "1100" => display2 <= "0110001"; --C:31
82      WHEN "1101" => display2 <= "1000010"; --D:42
83      WHEN "1110" => display2 <= "0110000"; --E:30
84      WHEN "1111" => display2 <= "0111000"; --F:38
85      WHEN OTHERS => display2 <= "0000000";
86  END CASE;
87
88  CASE ori3 IS
89      WHEN "0000" => display3 <= "0000001"; --0:01
90      WHEN "0001" => display3 <= "1001111"; --1:4F
91      WHEN "0010" => display3 <= "0010010"; --2:12
92      WHEN "0011" => display3 <= "0000110"; --3:06
93      WHEN "0100" => display3 <= "1001100"; --4:4C
94      WHEN "0101" => display3 <= "0100100"; --5:24
95      WHEN "0110" => display3 <= "0100000"; --6:20
96      WHEN "0111" => display3 <= "0001111"; --7:0F
97      WHEN "1000" => display3 <= "0000000"; --8:00
98      WHEN "1001" => display3 <= "0000100"; --9:04
99      WHEN "1010" => display3 <= "0001000"; --A:08
100     WHEN "1011" => display3 <= "1100000"; --B:60
101     WHEN "1100" => display3 <= "0110001"; --C:31
102     WHEN "1101" => display3 <= "1000010"; --D:42
103     WHEN "1110" => display3 <= "0110000"; --E:30
104     WHEN "1111" => display3 <= "0111000"; --F:38
105     WHEN OTHERS => display3 <= "0000000";
106  END CASE;
107  END PROCESS;
108
109  END hex_disp_architecture;

```